

# Evan Noyes and Henry Gridley Lab Report 10

## **Assignment 1**

a)

 


b)

 


Every 1000 clock cycles the system produces a pulse with a width of 75 cycles, the default specified by the counter. This width is changed when signals are given to the inputs

# **Assignment 2**

a)

 

b)

 

Here you can see the pulse cycles in the middle row, which will remain at a constant width since there is no input

c)

#### Before pulse:

- 0 => 1 Transition: 1.2012
- 1 => 0 Transition: 1.2088
- Total Width: 76 cycles

#### After pulse:

0 => 1 Transition: 1.3013
1 => 0 Transition: 1.3095
Total Width: 82 cycles

We see a +6 increase in pulse width, consistent with the increment on our counter

d)

#### Before pulse:

0 => 1 Transition: 1.2012
1 => 0 Transition: 1.2088
Total Width: 76 cycles

#### After pulse:

0 => 1 Transition: 1.3013
1 => 0 Transition: 1.3083
Total Width: 70 cycles

We see a **-6 decrease** in pulse width, consistent with the increment on our counter

### **Assignment 3**

